

# Chapter E5: Voltage

## E5.2 Resistance and Ohm's Law

Two important ideas from previous chapters:

$$|\Delta\mathcal{V}_b| = |\Delta\mathcal{V}_{\text{wire}}| = E_{\text{wire}}L, \quad (1)$$

and

$$\vec{J} = \sigma\vec{E}. \quad (2)$$

We can use this to relate the current  $I = JA$  to the voltage difference of a battery. We define the resistance of an object by:

$$R \equiv \frac{|\Delta\mathcal{V}|}{I}. \quad (3)$$

If the  $R$  of some object is constant as  $I$  varies, then we say that the object is *ohmic*. Note: many objects aren't ohmic.

For a wire of length  $L$ , uniform thickness  $A$  and constant conductivity  $\sigma$ ,

$$R = \frac{L}{\sigma A}. \quad (4)$$

## E5.3 Two Wires in Series

For objects in a circuit in series,

$$I = I_1 = I_2 = I_3 \dots, \quad (5)$$

and

$$|\Delta\mathcal{V}_b| = |\Delta\mathcal{V}_1| + |\Delta\mathcal{V}_2| + |\Delta\mathcal{V}_3| + \dots, \quad (6)$$

where  $I_n$  is the current through the  $n^{\text{th}}$  object and  $|\Delta\mathcal{V}_n|$  is the potential difference across the  $n^{\text{th}}$  object. You should understand why these equations have to be true.

## E5.4 Total Resistance in a Series Circuit

An immediate consequence of the above two equations is that the total resistance in a series circuit is given by:

$$R_{\text{tot}} = R_1 + R_2 + R_3 + \dots, \quad (7)$$

where  $R_n$  is the resistance of the  $n^{\text{th}}$  object.

### **E5.5 The Voltage at a Point**

To speak about the voltage at a point, as opposed to the voltage difference between two points, it is necessary to fix some reference point as  $\mathcal{V} = 0$ .

### **E5.7 Electrical Power**

The electrical power dissipated in a circuit is given by

$$P = |\Delta\mathcal{V}|I . \tag{8}$$

The unit of power is the Watt ( $1 \text{ W} = 1\text{J/s}$ ). A frequently-used unit of energy is the kilowatt hour.

### **Examples:**

1. Your bathtub holds .8 cubic meters of water. It takes 10 minutes to fill up the tub. Assuming a constant flow rate, what is the current (of water) into the tub? If the round faucet is 5cm long and has a radius of 1 cm, what is the current density?