

## Chapter E6: Analyzing Circuits

### E6.2 Circuit Diagrams

Circuit diagrams are a useful and handy mental unwrappings of real circuits.

### E6.3 Circuit Elements in Parallel

The voltage difference across circuit elements in parallel are the same:

$$|\Delta\mathcal{V}_b| = |\Delta\mathcal{V}_1| = |\Delta\mathcal{V}_2| = |\Delta\mathcal{V}_3| = \dots , \quad (1)$$

where  $|\Delta\mathcal{V}_n|$  is the potential difference across the  $n^{\text{th}}$  object. You should understand why these equations have to be true.

The current, however, is *not* the same through all objects placed in a parallel circuit:

$$I_{\text{tot}} = I_1 + I_2 + \dots , \quad (2)$$

where  $I_n$  is the current flowing through the  $n^{\text{th}}$  object.

For a set of resistors in parallel, the following relationship holds:

$$\frac{1}{R_{\text{set}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots , \quad (3)$$

where  $R_n$  is the resistance of the  $n^{\text{th}}$  object.

### E6.4 Total Resistance in a Series Circuit

Repeatedly apply the basic equations for series and parallel circuits. Working neatly and using lots of space will help.

### E6.5 Electrical Safety Issues

Current is bad for you.

## Circuit Summary

The **potential difference** between two points in a circuit measures change in potential energy per unit charge between these two points. Potential difference is measured in volts; one Volt is one Joule per Coulomb.

The **EMF** of a battery is a property of the battery. It measures the potential energy per charge delivered by the battery. Its units are also volts. A battery's EMF doesn't depend on the sort of circuit hooked up to it.

**Current** is measured in Amps. One Amp = One Coulomb per second. The current at a point measures how much charge is flowing by per unit time.

An object's **resistance** is defined via  $R \equiv V/I$ , where  $V$  is the voltage drop across that object. If  $R$  is independent of  $V$  and  $I$ , we say that the object is ohmic. The unit of resistance is the Ohm. One Ohm ( $\Omega$ ) = One Volt per Amp.

### Series Circuit

$$\Delta\mathcal{V}_1 + \Delta\mathcal{V}_2 = \Delta\mathcal{V}_{\text{total}} . \quad (4)$$

$$I_1 = I_2 = I_{\text{total}} . \quad (5)$$

$$R_1 + R_2 = R_{\text{total}} . \quad (6)$$

### Parallel Circuit

$$\Delta\mathcal{V}_1 = \Delta\mathcal{V}_2 = \Delta\mathcal{V}_{\text{total}} . \quad (7)$$

$$I_1 + I_2 = I_{\text{total}} . \quad (8)$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{\text{total}}} . \quad (9)$$

Except for Eq. (9), these equations should be "obvious," in that they should be viewed as logical and inevitable consequences of the definitions of  $V$  and  $I$  and the conservation of energy and charge.

## Practice

For the circuit drawn below, calculate the voltage drop across, and the current flowing through each resistor.